

ECE 164 – Analog Integrated Circuit Design

Sensor Interface Redesign
Triton Industries, Inc.


December 3rd, 2023

Jason Smyslov PID: A17132126
jsmyslov@ucsd.edu

Michael Hawkins PID: A17234954
mjhawkins@ucsd.edu

Professor: Drew Hall

Design Outline

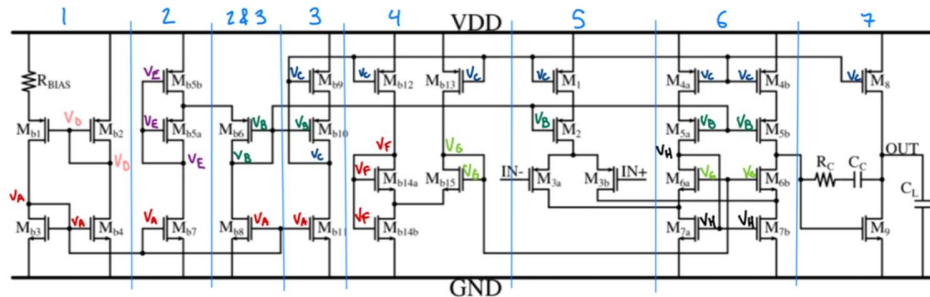

To properly re-design the sensor interface, we initially broke the circuit up into subcircuits with specific characteristics and functions covered in lectures. These subcircuits were: Constant G_m (1), Current Mirror Bias (2, 3, 4), Folded Cascode (5,6), Compensation Network (7), and a Common Source amplifier (7). Most of our components are MOSFETs, so MATLAB scripts with parameters of MOSFET equations like overdrive voltage and drain current were created.

Values for k_n' , k_p' , and λ were taken from the homework for calculations. Initially, we designed each circuit to meet a V_{ov} of 200 mV for every transistor to meet specifications and give enough room to keep all transistors in saturation. Additionally, we made some assumptions such as setting every V_t to 400 mV and every length to $1\mu\text{m}$ to standardize calculations. As we proceeded to the CS amplifier, we decided on setting the output to 900 mV to keep both transistors in saturation. Afterwards, we calculated g_{m9} using our desired phase margin and gain bandwidth. From this we determined the approximate current for the corresponding g_m and started sizing the CS amplifier accordingly.

Then we began to size the Folded Cascode circuit and Current Mirror Bias circuit to meet the voltages needed for the CS amplifier. In particular, we chose voltages at nodes that would keep with the 200 mV overdrive voltage and limit the V_{ds} in case we would need to correct for currents later. We also took into consideration that some widths would need to be larger in order to achieve parameters for mirroring, so we preemptively raised widths for mirrored transistors connected to the CS amplifier. This was because we found that our $\frac{W}{L}$ ratios calculated in the CS amplifier were quite large and would get larger when optimizing.

For the constant G_m circuit, we wanted to size the two lengths within a ratio and ensure that the voltage from the circuit would keep the Current Mirror Bias circuit M_{b7} , M_{b8} , and M_{b11} within saturation. We verified the operation of the constant G_m circuit and began to optimize the circuit by raising widths for transistors M_9 , M_8 , and lowered M_3 until parameters were reached and power dissipation was lowered.

Schematic

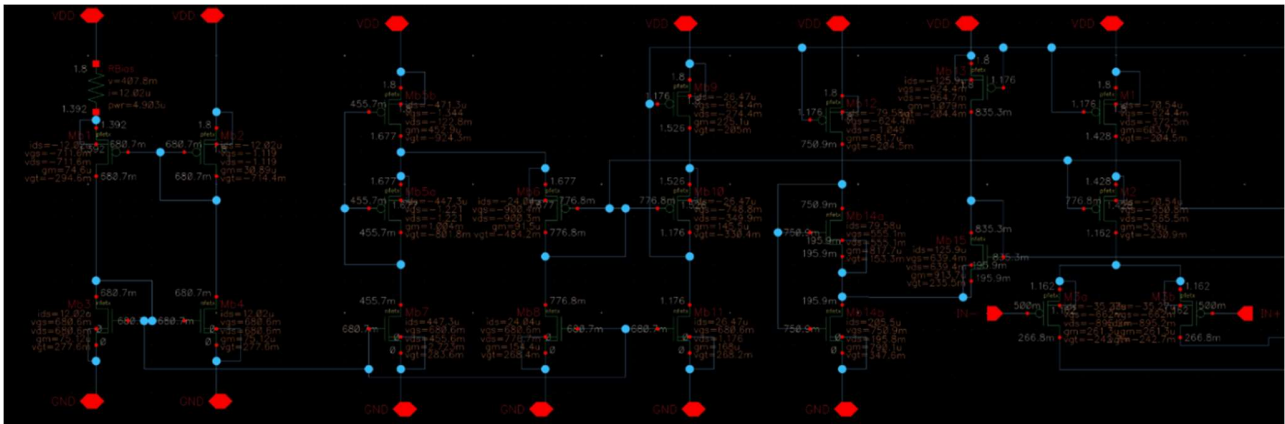


Figure1: Left Side of Design Circuit (Currents, Vov, Node Voltages)

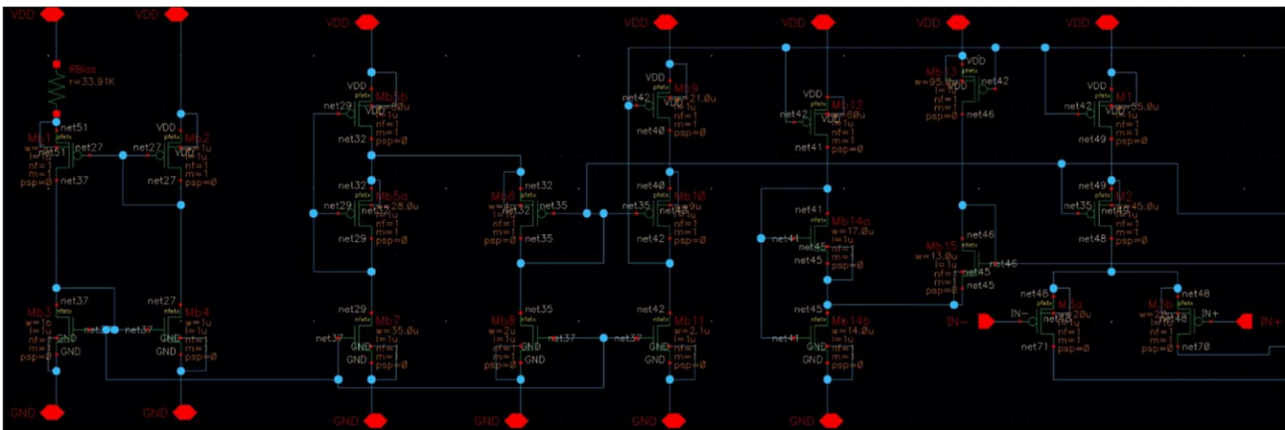


Figure2: Left Side of Design Circuit (W/L, R)

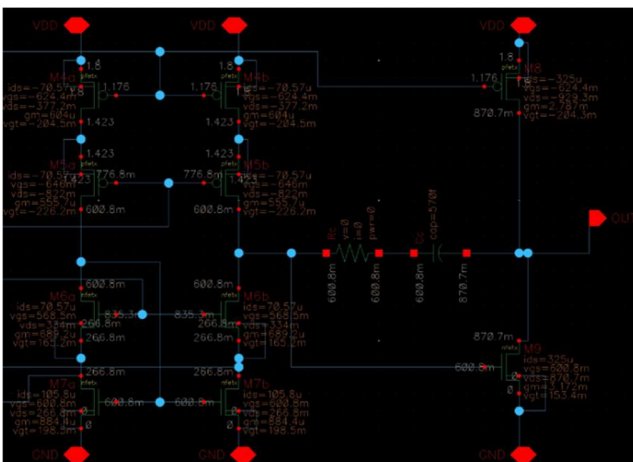
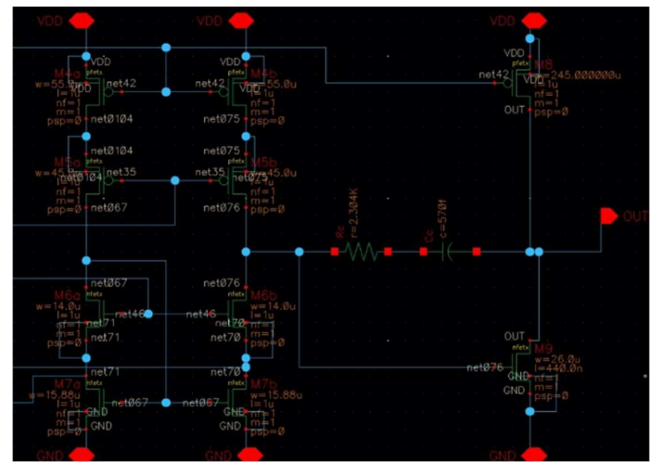
 
Figure3: Right Side of Design Circuit
(Currents, Vov, Node Voltages)

Figure4: Right Side of Design Circuit (W/L)

Common Source & Compensation Network



$$A_{dc} = A_{v1} A_{v2} = g_{mcb} R_1 g_{mq} R_2$$

$$\omega_{p1} \approx -\frac{1}{C_c g_{mq} R_2 R_1} \quad \omega_c = \text{GBW} = \omega_{p1} A_v = \frac{g_{mcb}}{C_c}$$

$$\omega_{p2} = -\frac{g_{mq}}{C_2} \quad \text{PM} = 90^\circ - \tan^{-1}\left(\frac{\omega_c}{\omega_{p2}}\right)$$

$$C = 550 \text{ f}$$

$$\text{PM} = 65^\circ$$

$$\text{Unity Gain BW} = 60 \text{ MHz}$$

$$\omega_{p2} = \frac{60 \text{ MHz} \times 2\pi}{\tan(25^\circ)} = 808.46 \text{ E6 rad/s}$$

$$g_{mq} = \omega_{p2} \cdot C_2 = 808.46 \text{ E6} \times 5 \times 10^{-12} = 4.04 \text{ mS}$$

$$V_{ov} = 200 \text{ mV}$$

$$K = 20$$

$$I_{D_{Mq}} = \frac{g_{mq} V_{ov}}{2} = 404.23 \text{ } \mu\text{A}$$

$$I_{M_{GB}} = I_{D_c} / K = 404.23 \text{ } \mu\text{A} / 20 = 20.21 \text{ } \mu\text{A}$$

$$I_D = \frac{1}{2} k_n' \left(\frac{W}{L}\right) V_{ov}^2 (1 + \lambda V_{DS})$$

$$\lambda = .1 \quad V_{DS} = .9 \text{ V}$$

$$\Rightarrow \left(\frac{W}{L}\right) = \frac{2 I_{Dq}}{k_n' V_{ov}^2 (1 + \lambda V_{DS})}$$

$$\Rightarrow \frac{2 (404.23 \text{ } \mu\text{A})}{(270 \text{ } \mu\text{A/V}^2) (.2)^2 (1 + .1 \times .9)} = 68.68$$

$$\begin{aligned} W_q &= 31 \text{ } \mu \\ L_q &= .45 \text{ } \mu \end{aligned} \quad \left(\frac{W}{L}\right)_q = 68$$

$$\begin{aligned} \omega_{p1} &= \frac{1}{C_c g_{mq} R_2 R_1} \\ &= \frac{1}{(5 \times 10^{-12}) (4.04 \text{ mS}) (24.738 \text{ k}) (494.8 \text{ k})} \\ &= 4.0444 \text{ E3 rad/s} \end{aligned}$$

$$R_2 = \frac{1}{\lambda I_{Dq}} = \frac{1}{.1 \cdot (404.23 \text{ } \mu\text{A})} = 24.738 \text{ k}\Omega$$

$$R_1 = \frac{1}{\lambda I_{missor}} = \frac{1}{.1 (20.21 \text{ } \mu\text{A})} = 494.8 \text{ k}\Omega$$

$$g_{mcb} = \frac{2 (20.21 \text{ } \mu\text{A})}{.2} = 202.1 \text{ } \mu\text{S}$$

$$A_{V_1} = g_{m_{c6}} R_1 = (202.1 \mu S)(494.8 k\Omega) = 100 \approx 40 \text{ dB}$$

$$\text{Power} \leq 2.5 \text{ mW}$$

$$A_{V_2} = g_{m_q} R_2 = (4.04 \text{ mS})(24.738 k\Omega) = 100 \approx 40 \text{ dB}$$

$$\rightarrow I_{\text{tot}} = \frac{P}{V} = \frac{2.5 \text{ mW}}{1.8 \text{ V}} = 1.38 \text{ mA}$$

$$A_V = A_{V_1} A_{V_2} = 40 + 40 = 80 \text{ dB} \approx 65 \text{ dB} \checkmark$$

$$\rightarrow I_{\text{tot}} \leq 1.39 \text{ mA}$$

$$\text{aiming for } \rightarrow I_{\text{tot}} \leq 1.25 \text{ mA}$$

$$\approx 10\% \text{ guardband}$$

$$PM = 90^\circ - \tan^{-1} \left(\frac{\omega_c}{\omega_{p_2}} \right)$$

$$65^\circ = 90^\circ - \tan^{-1} \left(\frac{\omega_c}{808.46 \text{ rad/s}} \right)$$

$$\tan(25^\circ) = \frac{\omega_c}{808.46 \text{ rad/s}}$$

$$\omega_c = 60 \text{ MHz}$$




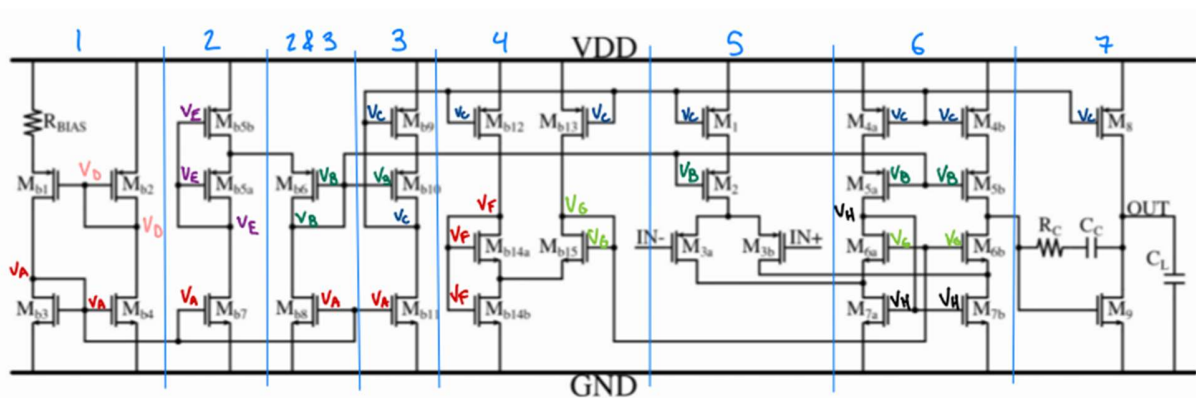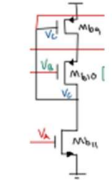

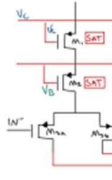
 


Figure 1 – Amplifier architecture

Spec	Hand Calc	Sim	Discrep
R_{BIAS}	32k	33.91k	6%
$(\omega_c)_{b1}$	5.68	5	1.3%
$(\omega_c)_{b2}$	1.04	1	4%
$(\omega_c)_{b3}$	1.04	1	4%
$(\omega_c)_{b4}$	1.04	1	4%

1	Mosfet Parameters	M1, M2, M3	1.2500e-05
2	kn = 267.2e-6; kp = 49.1e-6; lambda = .1;	M2, M3, M4	1.2500e-05
3	Voltages, Components	kn	2.6720e-04
4	Vdd = 1.8; Vtn = .43; Vtp = -.38;	kp	4.9100e-05
5		lambda	0.1000
6	Wise .7 Vds drop, 5-1 sizing ratio, Budget 12.5uA for R_bias, M1, M3	R_bias	3.2000e+04
7	Vov_Mb1 = .3; Vov_Mb3 = .3; Id_Mb1_Mb3 = 12.5e-6;	Vdd	1.8000
8	Budget 12.5uA for M2, M4	Vb1, Mb1	0
9	Vov_Mb2 = .7; Vov_Mb4 = .3; Id_Mb2_Mb4 = 12.5e-6;	Vb1, Mb2	0
10	R_bias = (Vdd - 2*.7) / Id_Mb1_Mb3;	Vb1, Mb3	0
11	Neglecting Channel length to simplify calculations, so Vds = 0	Vb1, Mb4	0
12	Vds_Mb1 = 0; Vds_Mb2 = 0; Vds_Mb3 = 0; Vds_Mb4 = 0;	Vov_Mb1	0.3000
13	W1_Mb1 = (2*Id_Mb1_Mb3)/(kp*Vov_Mb1*2*(1+lambda*Vds_Mb1));	Vov_Mb2	0.7000
14	W1_Mb2 = (2*Id_Mb2_Mb4)/(kp*Vov_Mb2*2*(1+lambda*Vds_Mb2));	Vov_Mb3	0.3000
15	W1_Mb3 = (2*Id_Mb1_Mb3)/(kn*Vov_Mb3*2*(1+lambda*Vds_Mb3));	Vov_Mb4	0.3000
16	W1_Mb4 = (2*Id_Mb2_Mb4)/(kn*Vov_Mb4*2*(1+lambda*Vds_Mb4));	Vtn	0.4300
		Vtp	0.3800
		W1, Mb1	5.6574
		W1, Mb2	1.0391
		W1, Mb3	1.0396
		W1, Mb4	1.0396

			Spec	Hand Calc	Sim	Discrep
	<pre> 1 %Budgetting 475uA for Current in Mb5b 2 %Budgetting 450uA for Current in Mb5a, Mb7 3 %Mosfet Parameters 4 kn = 267.2e-6; kp = 49.1e-6; lambda = .1; 5 %Voltages, Components 6 Vdd = 1.8; Vtn = .43; Vtp = .38; 7 Vov_Mb7 = .3; Vov_Mb5a = .8; Vov_Mb5b = .9; 8 Id_Mb5a_Mb7 = 450e-6; Id_Mb5b = 475e-6; 9 %Neglecting Channel length to simplify calculations, so Vds = 0 10 %besides Mb5b because of triode 11 Vds_Mb5b = 0.125; Vds_Mb5a = 0; Vds_Mb7 = 0; 12 13 WL_Mb7 = (2*Id_Mb5a_Mb7)/(kn*Vov_Mb7^2*(1+lambda*Vds_Mb7)); 14 WL_Mb5a = (2*Id_Mb5a_Mb7)/(kp*Vov_Mb5a^2*(1+lambda*Vds_Mb5a)); 15 WL_Mb5b = Id_Mb5b/(kp*(Vov_Mb5b*Vds_Mb5b - .5*Vds_Mb5b^2)); </pre>	<pre> Id_Mb5a_Mb7 4.5000e-04 Id_Mb5b 4.7500e-04 kn 2.6720e-04 kp 4.9100e-05 lambda 0.1000 Vdd 1.8000 Vds_Mb5a 0 Vds_Mb5b 0.1250 Vds_Mb7 0 Vov_Mb5a 0.8000 Vov_Mb5b 0.9000 Vov_Mb7 0.3000 Vtn 0.4300 Vtp 0.3800 WL_Mb5a 28.6405 WL_Mb5b 92.4096 WL_Mb7 37.4251 </pre>	$(w/L)_{b5a}$	28.64	28	2.3%
			$(w/L)_{b5b}$	92.41	80	15.5%
			$(w/L)_{b7}$	37.43	35	6.9%
	<pre> 7 %Budgetting 25uA for Current in Mb6, Mb8 8 Vov_Mb6 = .48; Vov_Mb8 = .27; Id_Mb6_Mb8 = 24e-6; 9 %Neglecting Channel length to simplify calculations, so Vds = 0 10 Vds_Mb6 = 0; Vds_Mb8 = 0; 11 12 WL_Mb6 = (2*Id_Mb6_Mb8)/(kn*Vov_Mb6^2*(1+lambda*Vds_Mb6)); 13 WL_Mb8 = (2*Id_Mb6_Mb8)/(kp*Vov_Mb8^2*(1+lambda*Vds_Mb8)); </pre>	<pre> Vov_Mb6 0.4800 Vov_Mb8 0.2700 Vtn 0.4300 Vtp 0.3800 WL_Mb6 3.8895 WL_Mb8 2.2589 </pre>	$(w/L)_{b6}$	3.89	4	2.8%
			$(w/L)_{b8}$	2.26	2	13%
	<pre> 9 %Budgetting 25uA for Current in Mb9, Mb10, Mb11 10 Vov_Mb9 = .21; Vov_Mb10 = .33; Vov_Mb11 = .27; Id_Mb9_Mb11 = 26e-6; 11 %Neglecting Channel length to simplify calculations, so Vds = 0 12 Vds_Mb9 = 0; Vds_Mb10 = 0; Vds_Mb11 = 0; 13 14 WL_Mb9 = (2*Id_Mb9_Mb11)/(kp*Vov_Mb9^2*(1+lambda*Vds_Mb9)); 15 WL_Mb10 = (2*Id_Mb9_Mb11)/(kp*Vov_Mb10^2*(1+lambda*Vds_Mb10)); 16 WL_Mb11 = (2*Id_Mb9_Mb11)/(kn*Vov_Mb11^2*(1+lambda*Vds_Mb11)); </pre>	<pre> Vov_Mb9 0.3300 Vov_Mb10 0.2700 Vov_Mb11 0.2100 Vtn 0.4300 Vtp 0.3800 WL_Mb9 8.6030 WL_Mb10 2.3615 WL_Mb11 21.2441 </pre>	$(w/L)_{b9}$	21.2	21	1%
			$(w/L)_{b10}$	8.6	9	4.4%
			$(w/L)_{b11}$	2.36	2.1	12.4%
	<pre> 8 %Budgetting 75uA for Current in Mb12, Mb14a 9 %Budgetting 125uA for Current in Mb13, Mb15a -> 200u in Mb14b 10 Vov_Mb12 = .21; Vov_Mb14a = .16; Id_Mb12_Mb14a = 75e-6; 11 Vov_Mb13 = .21; Vov_Mb15 = .23; Id_Mb13_Mb15 = 125e-6; 12 Vov_Mb14b = .35; Id_Mb14b = 200e-6; Vds_Mb14b = .2; 13 %Neglecting Channel length to simplify calculations, so Vds = 0 14 Vds_Mb12 = 0; Vds_Mb13 = 0; Vds_Mb14a = 0; Vds_Mb15 = 0; 15 16 WL_Mb12 = (2*Id_Mb12_Mb14a)/(kp*Vov_Mb12^2*(1+lambda*Vds_Mb12)); 17 WL_Mb13 = (2*Id_Mb13_Mb15)/(kp*Vov_Mb13^2*(1+lambda*Vds_Mb13)); 18 WL_Mb14a = (2*Id_Mb12_Mb14a)/(kn*Vov_Mb14a^2*(1+lambda*Vds_Mb14a)); 19 WL_Mb15 = (2*Id_Mb13_Mb15)/(kn*Vov_Mb15^2*(1+lambda*Vds_Mb15)); 20 WL_Mb14b = Id_Mb14b/(kn*(Vov_Mb14b*Vds_Mb14b - .5*Vds_Mb14b^2)); </pre>	<pre> Vov_Mb12 0.2100 Vov_Mb13 0.2100 Vov_Mb14a 0.1600 Vov_Mb14b 0.3500 Vov_Mb15 0.2300 Vtn 0.4300 Vtp 0.3800 WL_Mb12 60.0376 WL_Mb13 96.9838 WL_Mb14a 19.0050 WL_Mb14b 14.9701 WL_Mb15 14.8569 </pre>	$(w/L)_{b12}$	60	60	0%
			$(w/L)_{b13}$	97	95	2.1%
			$(w/L)_{b14a}$	19	17	11.8%
			$(w/L)_{b14b}$	15	14	7.1%
			$(w/L)_{b15}$	14.9	13	14.6%
	<pre> 8 %Budgetting 70uA for Current in M1, M2 9 %Budgetting 35uA for Current in M3a, M3b 10 Vov_M1 = .21; Vov_M2 = .23; Id_M1_M2 = 70e-6; 11 Vov_M3a = .25; Vov_M3b = .25; Id_M3a_M3b = 35e-6; 12 %Neglecting Channel length to simplify calculations, so Vds = 0 13 Vds_M1 = 0; Vds_M2 = 0; Vds_M3a = 0; Vds_M3b = 0; 14 15 WL_M1 = (2*Id_M1_M2)/(kp*Vov_M1^2*(1+lambda*Vds_M1)); 16 WL_M2 = (2*Id_M1_M2)/(kp*Vov_M2^2*(1+lambda*Vds_M2)); 17 WL_M3a = (2*Id_M3a_M3b)/(kp*Vov_M3a^2*(1+lambda*Vds_M3a)); 18 WL_M3b = (2*Id_M3a_M3b)/(kp*Vov_M3b^2*(1+lambda*Vds_M3b)); </pre>	<pre> Vov_Mb12 0.2100 Vov_Mb13 0.2100 Vov_Mb14a 0.1600 Vov_Mb14b 0.3500 Vov_Mb15 0.2300 Vtn 0.4300 Vtp 0.3800 WL_Mb12 60.0376 WL_Mb13 96.9838 WL_Mb14a 19.0050 WL_Mb14b 14.9701 WL_Mb15 14.8569 </pre>	$(w/L)_{M1}$	64.7	55	17.6%
			$(w/L)_{M2}$	53.9	45	19.8%
			$(w/L)_{3A}$	22.8	20	14%
			$(w/L)_{3B}$	22.8	20	14%




```

8 %Budgetting 700A for Current in M4a, M4a, M5a, M5b, M6a, M6b
9 %Budgetting 105uA for Current in M7a, M7b
10 Vov_M4a = .21; Vov_M4b = .21; Vov_M5a = .23; Vov_M5b = .23;
11 Vov_M6a = .17; Vov_M6b = .17; Id_M4a_M6b = 75e-6;
12 Vov_M7a = .2; Vov_M7b = .2; Id_M7a_M7b = 105e-6;
13 %Neglecting Channel length to simplify calculations, so Vds = 0
14 Vds_M4a = 0; Vds_M4b = 0; Vds_M5a = 0; Vds_M5b = 0;
15 Vds_M6a = 0; Vds_M6b = 0; Vds_M7a = 0; Vds_M7b = 0;
16
17 Wt_M4a = (2*Id_M4a_M6b)/(kp*Vov_M4a^2*(1+lambda*Vds_M4a));
18 Wt_M4b = (2*Id_M4a_M6b)/(kp*Vov_M4b^2*(1+lambda*Vds_M4b));
19 Wt_M5a = (2*Id_M4a_M6b)/(kp*Vov_M5a^2*(1+lambda*Vds_M5a));
20 Wt_M5b = (2*Id_M4a_M6b)/(kp*Vov_M5b^2*(1+lambda*Vds_M5b));
21 Wt_M6a = (2*Id_M4a_M6b)/(kn*Vov_M6a^2*(1+lambda*Vds_M6a));
22 Wt_M6b = (2*Id_M4a_M6b)/(kn*Vov_M6b^2*(1+lambda*Vds_M6b));
23 Wt_M7a = (2*Id_M7a_M7b)/(kn*Vov_M7a^2*(1+lambda*Vds_M7a));
24 Wt_M7b = (2*Id_M7a_M7b)/(kn*Vov_M7b^2*(1+lambda*Vds_M7b));

```

Vov_M4a	0.2100
Vov_M4b	0.2100
Vov_M5a	0.2300
Vov_M5b	0.2300
Vov_M6a	0.1700
Vov_M6b	0.1700
Vov_M7a	0.2000
Vov_M7b	0.2000
Vtn	0.4300
Vtp	0.3800
Wt_M4a	55.4193
Wt_M4b	55.4193
Wt_M5a	46.2002
Wt_M5b	46.2002
Wt_M6a	15.5399
Wt_M6b	15.5399
Wt_M7a	17.7769
Wt_M7b	17.7769

Spec	Hand Calc	Sim	Discrep
$(W/L)_{4A, 4B}$	55.4	55	.7%
$(W/L)_{5A, 5B}$	46.2	45	2.7%
$(W/L)_{6A, 6B}$	15.5	14	10.7%
$(W/L)_{7A, 7B}$	17.8	15.88	12.1%

 

```

8 %Budgetting 325uA for Current in M8, M9
9 Vov_M8 = .2; Vov_M9 = .16; Id_M8_M9 = 325e-6;
10
11 %Neglecting Channel length to simplify calculations, so Vds = 0
12 Vds_M8 = 0; Vds_M9 = 0;
13
14 Wt_M8 = (2*Id_M8_M9)/(kp*Vov_M8^2*(1+lambda*Vds_M8));
15 Wt_M9 = (2*Id_M8_M9)/(kn*Vov_M9^2*(1+lambda*Vds_M9));

```

Vds_M8	0
Vds_M9	0
Vov_M8	0.2000
Vov_M9	0.1600
Vtn	0.4300
Vtp	0.3800
Wt_M8	239.3075
Wt_M9	68.7102

Spec	Hand Calc	Sim	Discrep
$(W/L)_{M8}$	239.3	245	.2%
$(W/L)_{M9}$	69	$\frac{26}{.44} = 59$	16.9%

$$\begin{aligned}
 I_{tot} &= I_{DM3} + I_{DM4} + I_{DM7} + I_{DM9} + I_{DM11} + I_{DM14B} + I_{DM7A} + I_{DM7B} + I_{DM9} \\
 &= 12.5\mu A + 12.5\mu A + 450\mu A + 24\mu A + 26\mu A + 200\mu A + 105\mu A + 105\mu A + 329\mu A \\
 &= 1.26\text{ mA} \quad P = 1.26\text{ mA} \cdot 1.8\text{ V} = 2.268\text{ mW}
 \end{aligned}$$

Spec	Hand Calculation	Simulation	Discrepancy
Phase Margin	65°	66.14°	+1.14°
Gain Margin	—	15.78 dB	—
DC Gain	80 dB	79.72 dB	-0.28 dB
Unity Gain Bandwidth	60 MHz	61.39 MHz	+1.39 MHz
Power Dissipation	2.268 mW	2.275 mW	+7 μW

Bode Plot

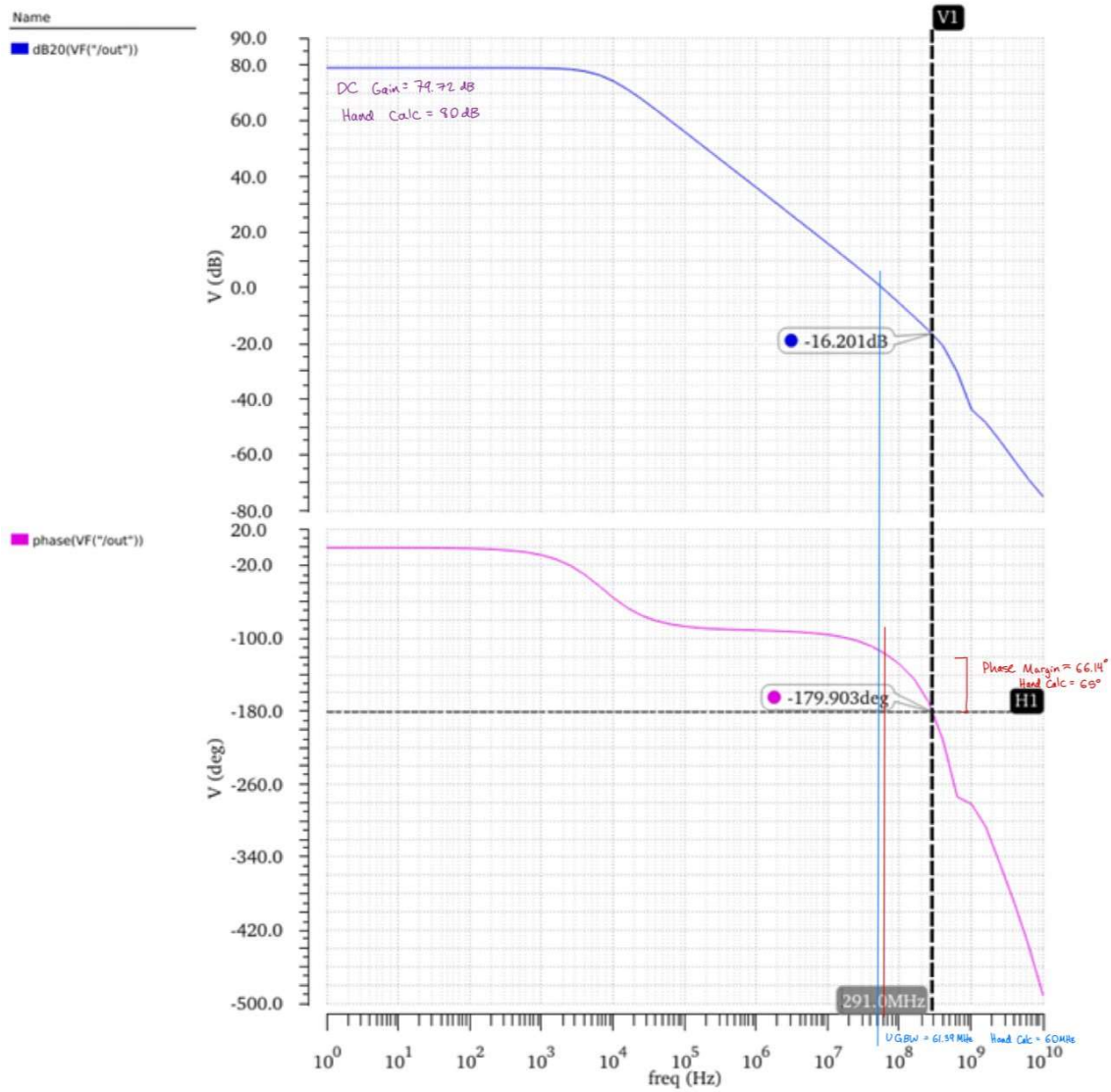


Figure4: Bode Plot Simulation

1	dB20(VF("/out"))	wave	<input checked="" type="checkbox"/>	<input type="checkbox"/>
2	phase(VF("/out"))	wave	<input checked="" type="checkbox"/>	<input type="checkbox"/>
3	phaseMargin(VF("/out"))	65.22	<input checked="" type="checkbox"/>	<input type="checkbox"/>
4	gainMargin(VF("/out"))	-16.21	<input checked="" type="checkbox"/>	<input type="checkbox"/>
5	gainBwProd(VF("/out"))	66.48M	<input checked="" type="checkbox"/>	<input type="checkbox"/>
6	unityGainFreq(VF("/out"))	60.77M	<input checked="" type="checkbox"/>	<input type="checkbox"/>
7	bandwidth(VF("/out")) 3 "low"	7.13K	<input checked="" type="checkbox"/>	<input type="checkbox"/>
8	dB20(value(VF("/out")) 0)	79.37	<input checked="" type="checkbox"/>	<input type="checkbox"/>
9	(VDC("/vdd") * IDC("/V3/PLUS") * -1)	2.275m	<input checked="" type="checkbox"/>	<input type="checkbox"/>
10	V3/PLUS		<input type="checkbox"/>	<input checked="" type="checkbox"/>

Transient Simulation

 


Figure5: Input Transient Simulation

 


Figure6: Output Transient Simulation

These graphs are based on differential inputs of $2.5 \mu\text{V}_\text{P}$ and $-2.5 \mu\text{V}_\text{P}$ using a sine wave source (Figure5). This source was used because we wanted to view the differential voltage across the sensor interface we created. To accomplish this, we needed to half the voltage coming into each side and place a negative voltage for the negative input. This voltage simulated a $10 \mu\text{V}_\text{PP}$ sine wave on the input and the resulting output is in figure 6. Placing a $5 \mu\text{V}$ source in a common mode configuration would yield us a similar type of result, however the magnitude of the final graph would not be as significant. Since we are using a sensor interface, we believe that the differential mode analysis of the transient response would be more beneficial as a result and is posted above.

Comments & Conclusions

The project followed quite closely to hand calculations for most of the project. However, for the project to be optimized properly, the project required V_{ovs} to be driven down to their limit of 150 mV. In order to accomplish this in the overall circuit we considered raising lengths for certain transistors to minimize the $\frac{W}{L}$ ratios and lower the widths of most transistors since the 'm' factor for mirroring transistors would soon be an issue. After this, we sized the transistors in the common source amplifier. We expected the voltage at the gate of the pMOS to increase and the widths and lengths of both transistors to increase. As of now, the nMOS in the common source amplifier is at the lowest voltage value to be within specifications for the given g_m value. Our circuit has some room to adjust on the AC specifications and could benefit from this, but it would require a lot of manipulation throughout the circuit.

The lessons we learned from this project was that hand calculations can only take you so far without making assumptions on values needed to solve. This was a logical step that significantly reduced the time it takes to get valuable results but also allowed us to make small changes faster. At a certain point, the width and length values of transistors would have to be non-integer values to maximize the lowest possible power output.

In order to make these changes, it seemed that parametric analysis was not a tool in order to iterate quickly. Also, the tool had caused a disk error as well as a rare malformed lock-stake issue which prevented one partner from using Cadence. This required extensive debugging through Piazza and using clsAdminTool and has yet to be resolved.